

# THE JIM WILLIAMS P A P E R S

## High-speed amplifiers with low offset and drift

Amplifiers designed for wide bandwidth or fast settling often exhibit inferior characteristics at dc—that is, high voltage, current offset, and drift. Used with care, the techniques described here let you build circuits that exhibit exemplary performance from dc to MHz.


Jim Williams, *Linear Technology Corp*

**O**ften, you must produce an amplifier circuit that has both the low offset of a dc amplifier and the wide bandwidth of a fast device. A number of techniques let you achieve such a result. Which method is best depends heavily on your application. Several circuits follow that you can study, build, and compare to determine what's best for you.

**Fig 1** shows a composite amplifier that consists of an LT1097 low-drift device ( $IC_1$ ) and an LT1191 high-speed amplifier ( $IC_2$ ). The overall circuit is a unity-gain inverter that has its summing node at the junction of the two 1-k $\Omega$  resistors.  $IC_1$  monitors this summing node, compares it to ground, and drives  $IC_2$ 's positive input to complete a dc-stabilizing loop around  $IC_2$ . The 100-k $\Omega$ -0.01- $\mu$ F time constant at  $IC_1$  limits the amplifier's response to low-frequency signals.  $IC_2$  handles


high-frequency inputs, whereas  $IC_1$  stabilizes the dc operating point. The 4.7-k $\Omega$ /220 $\Omega$  divider at  $IC_2$ 's input prevents excessive overdrive during startup. This circuit combines  $IC_1$ 's 35- $\mu$ V offset and 1.5- $\mu$ V/ $^{\circ}$ C drift with  $IC_2$ 's 450V/ $\mu$ sec slew rate and 90-MHz bandwidth. Bias current, dominated by  $IC_2$ , is about 500 nA.

**Fig 2** is similar, except that the sensing is differential, preserving access to both of the fast amplifier's inputs.  $IC_1$  measures the dc error at  $IC_2$ 's input terminals and biases  $IC_2$ 's offset pin to force the offset to within 50  $\mu$ V.  $IC_2$ 's offset-pin biasing arrangement always lets  $IC_1$  find the servo point. The 0.01- $\mu$ F capacitor rolls off  $IC_1$ 's gain at low frequencies, and  $IC_2$  han-

 

**Fig 1—An integrator ( $IC_1$ ) reduces the drift of a wideband amplifier ( $IC_2$ ) by applying a signal to the wideband amplifier's noninverting input. That signal holds the wideband amplifier's summing junction at ground.**

# THE JIM WILLIAMS P A P E R S

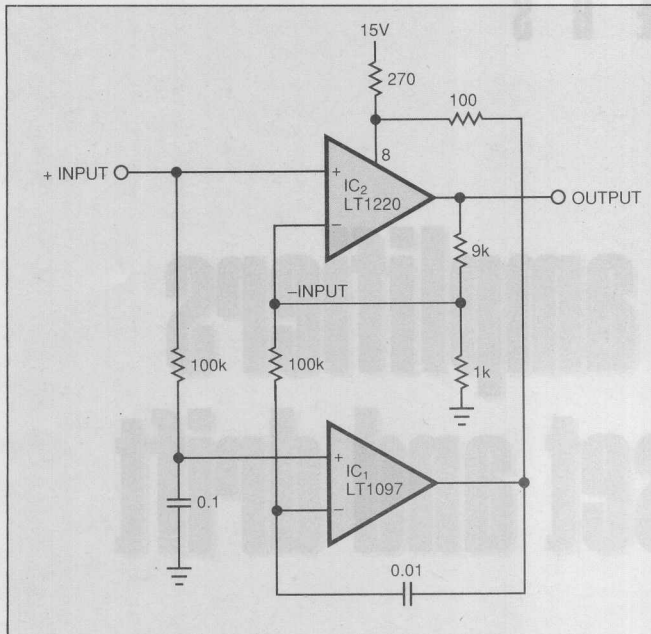

**Fig 2—**You can also stabilize the offset of a wideband amplifier ( $IC_2$ , in this case) by using a precision dc amplifier ( $IC_1$ ) to apply correcting signals to the wideband amplifier's offset-trim adjustment pin.

dles high-frequency signals. The combined characteristics of these amplifiers yield an offset voltage of 50  $\mu$ V, an offset drift of 1  $\mu$ V/ $^{\circ}$ C, a slew rate of 250 V/ $\mu$ sec, and a gain bandwidth of 45 MHz.


**Fig 3** shows wideband, highly stable gain-of-10 amplifier with high input impedance. The input capacitance is about 3 pF. Because of its low input capacitance and low (100 pA) bias current, the circuit is well

suited for use in probing IC wafers or as a pin amplifier in automatic-test systems.

$Q_1$  and  $Q_2$  constitute a simple, high-speed FET-input buffer.  $Q_1$  functions as a source follower, and the  $Q_2$  current-source load sets the drain-to-source channel current.  $IC_2$  provides a gain of 10 with 100-MHz bandwidth. Normally, this open-loop configuration would drift unacceptably because there is no dc feedback.  $IC_1$ , by comparing the filtered circuit output to a similarly filtered version of the input signal, provides the feedback to stabilize the circuit. The amplified difference between these signals sets  $Q_2$ 's bias—and hence  $Q_1$ 's channel current—thereby forcing  $Q_1$ 's  $V_{GS}$  to match the circuit's input and output potentials. The capacitor around  $IC_1$  provides stable loop compensation. The R-C network in  $IC_1$ 's output prevents that output from seeing high-speed edges coupled through  $Q_2$ 's collector-base junction.

**Fig 4a** shows a way to combine wide bandwidth with true differential inputs and dc stabilization.  $IC_1$  and  $IC_2$  sense the input differentially at gains of 10. Wideband amplifier  $IC_1$  feeds high-frequency signals to output amplifier  $IC_3$  via a highpass network. Low-frequency and dc information get to  $IC_3$  via the slower  $IC_2$ . The 2-k $\Omega$ /200-pF lowpass networks remove the input signal's high-frequency components, so only lower frequencies reach  $IC_2$ . Because the gain and bandwidth of the high- and low-frequency paths complement each other,  $IC_3$ 's output is an undistorted, amplified version of the input (see **Fig 4b**, trace D.)

**Fig 4b**, trace A is one side of a differential input signal applied to the circuit. Trace B is  $IC_1$ 's output

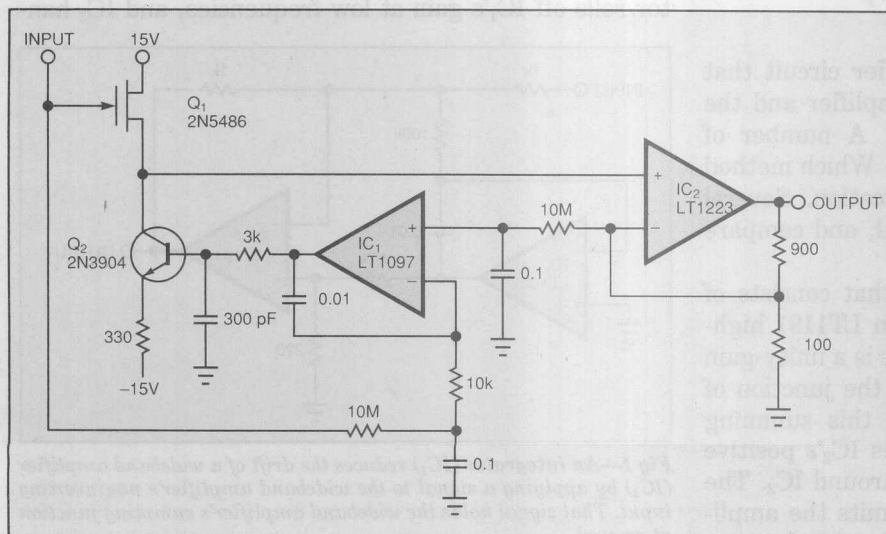

**Fig 3—**An integrator ( $IC_1$ ) drives a current source ( $Q_2$ ), which biases a FET ( $Q_1$ ) that completes a dc feedback loop around  $IC_2$  to stabilize the amplifier's operation at dc.

taken at the junction of the 500 $\Omega$  potentiometer and 0.001- $\mu$ F capacitor. Trace C is IC<sub>2</sub>'s output. With the "ac-gain" and "dc-gain-match" trims properly adjusted, the two paths' contributions match up and trace D is clean, with no residual artifacts. You can optimize the adjustments by trimming the ac gain for the squarest corners and the dc-gain match for a flat top. Bandwidth for this circuit exceeds 35 MHz; slew rate is 450V/ $\mu$ sec; and dc offset is about 200  $\mu$ V.

### Parallel paths yield the best of two worlds

Fig 5a shows a very powerful extension of the previous circuit. The circuits operate similarly, but this one has a gain of 1000; its bandwidth is about 35 MHz; its rise time is 7 nsec; and its delay is less than 7.5 nsec. Full-power response is available to 10 MHz, and broadband input noise is about 15  $\mu$ V. This kind of speed, coupled with true differential inputs, a gain of 1000, high dc stability, and low cost make the circuit broadly applicable in wideband instrumentation.

As before, two differential amplifiers, IC<sub>1</sub> and IC<sub>2</sub>, simultaneously sense the inputs. In this case, IC<sub>1</sub> is a 592-733 type operating at a gain of 100. Its differential outputs feed output amplifier IC<sub>3</sub> via 1- $\mu$ F/1-k $\Omega$  high-pass networks that strip out the dc content of IC<sub>1</sub>'s output. IC<sub>2</sub>, a precision dc differential amplifier, operates in similar fashion to its counterpart in the previous circuit, supplying dc and low-frequency information to IC<sub>3</sub> at a trimmed gain of 100.

In this case, the output amplifier, IC<sub>3</sub>, is not a follower but a differential-input/single-ended-output gain block whose nominal gain is 10. This change is necessary because IC<sub>1</sub>'s differential output must become a single-ended signal to provide the circuit's final output. Consequently, IC<sub>2</sub> does not directly apply its low-frequency information to IC<sub>3</sub> as it did before. Instead, IC<sub>4</sub> measures the difference between IC<sub>2</sub>'s output and a fraction of IC<sub>3</sub>'s output. IC<sub>4</sub>'s output, biasing IC<sub>3</sub>'s positive input via the 1-k $\Omega$  resistor, closes a loop around the circuit's dc and low-frequency path. To make the circuit's dc gain equal to its ac gain, you adjust the divider that feeds IC<sub>4</sub>'s negative input.

Fig 5b shows the circuit's response to a 60-nsec, 2.5-mV pulse, trace A. The  $\times 1000$  output, trace B, responds cleanly, with both delay and rise time in the 5- to 7-nsec range. Some small amount of overshoot is evident, but you can trim the overshoot with the peaking adjustment at IC<sub>1</sub>. Fig 5c plots the circuit's gain vs frequency. The gain is flat within 0.5 dB to 20 MHz, with the -3 dB point at 40 MHz. The overshoot of Fig 5b shows up here as a very slight gain increase starting around 1 MHz and continuing to about 15 MHz. The peaking adjustment eliminates this effect.

To use this circuit, apply a low-frequency or dc signal of known amplitude and adjust the low-frequency gain to  $\times 1000$  after the output has settled. Next, adjust the high-frequency gain so that the signal's leading and trailing corners have amplitudes identical to those

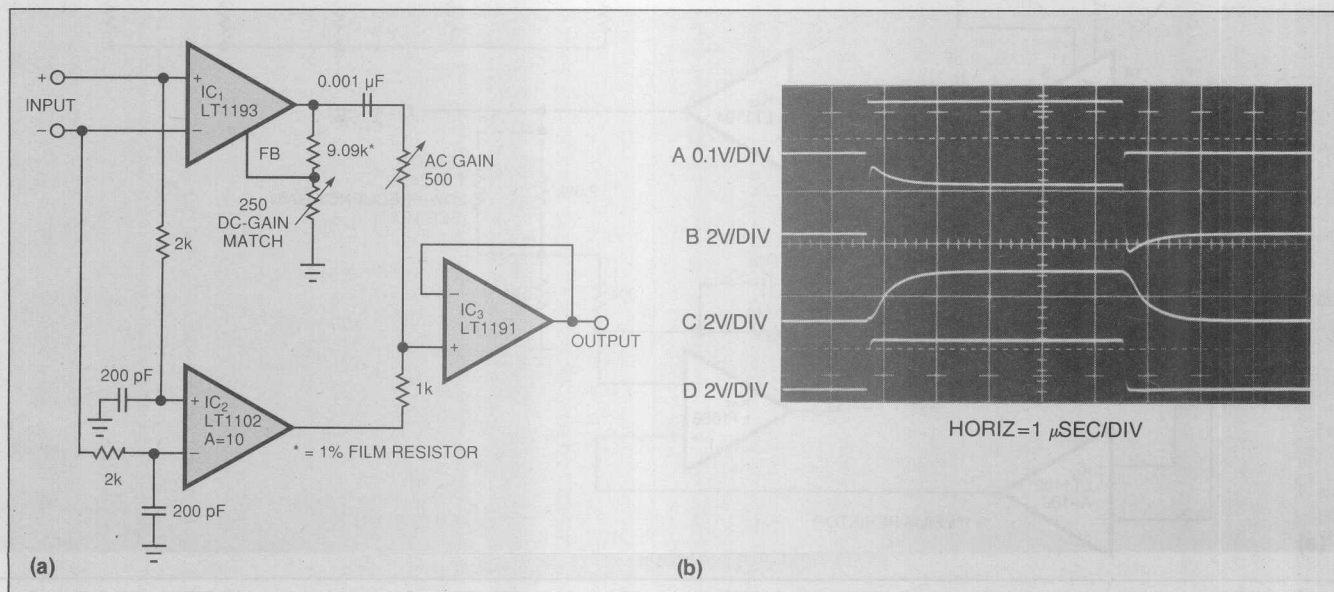


Fig 4—Parallel paths for ac and dc signals (a) provide low offset and good dynamic response—if you correctly adjust the trims (b, trace D).










ers in parallel with the chopper amplifiers provided good bandwidth. As **Figs 5e** and **5f** illustrate, these schemes have historically had a problem in many applications that demand the best at both dc and high frequencies: Unless you carefully match the dc and ac gains, the amplifiers' response to an input voltage step exhibits a long "tail." Keeping the response free of such tails over wide temperature ranges and long periods of time has always presented a challenge. Modern components make meeting that challenge easier, but the challenge still exists. **EDN**
     
## Author's biography

For more information on this article's author, turn to page 163 in the October 10, 1991, issue.

Article Interest Quotient (Circle One)  
High 473 Medium 474 Low 475



(c) as a slight peak near 6 MHz. In the other three photos, (d, e, and f), you see, respectively, the effects of correctly matching the ac and dc gains, setting the ac gain too high, and setting the dc gain too high.